

Reg. No .....

Name .....

**MSc DEGREE END SEMESTER EXAMINATION - OCTOBER 2019****SEMESTER 1 : PHYSICS****COURSE : 16P1PHYT04 : ELECTRONICS***(For Regular - 2019 Admission and Supplementary - 2016/2017/2018 Admissions)*

Time : Three Hours

Max. Marks: 75

**Section A****Answer any 5 (1 marks each)**

1. The differential gain is .....
  - a. very high
  - b. very low
  - c. dependent on input voltage
  - d. about 100
2. When a differential amplifier is operated single-ended, .....
  - a. the output is grounded
  - b. one input is grounded and signal is applied to the other
  - c. both inputs are connected together
  - d. the output is not inverted
3. Which of the following causes change in gain and phase shift?
  - a) All of the mentioned
  - b) Internally integrated inductors
  - c) Internally integrated Capacitor
  - d) Internally integrated Resistor
4. In op-amp, signal applied at inverting terminal appears at output terminal with a phase
  - a. 0
  - b. 90
  - c. 180
  - d. 45
5. Name the filter that has two stop bands?
  - a) Band-pass filter
  - b) Low pass filter
  - c) High pass filter
  - d) Band-reject filter

(1 x 5 = 5)

**Section B****Answer any 7 (2 marks each)**

6. Define input offset voltage and explain why it exists in all op-amps?
7. Define CMRR and explain its significance of large value of CMRR?
8. List two special cases of inverting amplifiers. Which one is most widely used and why?
9. Why is a resistor  $R_{OM}$  not needed in differential op-amp circuits?
10. Define break frequency and bandwidth?
11. Explain the effect of negative feedback on frequency response?

12. What are the major advantage and disadvantage of a single supply ac amplifier?
13. State two basic criteria required for oscillations in oscillators?
14. Design a high-pass filter at cutoff frequency of 1 kHz with a passband gain of 2. Also plot the frequency response curve.
15. What is a sample and hold circuit? Why is it needed?

(2 x 7 = 14)

### Section C

#### Answer any 4 (5 marks each)

16. The following specifications are given for a differential amplifier using two op-amps.  $R_1 = R_3 = 680 \Omega$ ,  $R_F = R_2 = 6.8 \text{ k}\Omega$ ,  $v_x = -1.5 \text{ V pp}$  and  $v_y = -2 \text{ V pp}$  sine waves at 1 kHz. The op-amp is 741c. Calculate (a) the voltage gain and the input resistance and (b) the output voltage of the amplifier. Assume that the output is initially nulled ( $V_{o0T} = 0\text{V}$ ).
17. Design a compensating network for the LM307 op-amp. Draw the circuit diagram. The op-amp uses  $\pm 10 \text{ V}$  supply voltages. (The input offset voltage specified in the data sheet for LM307 is 10 mV).
18. For an ac non inverting amplifier with a single power supply using IC 741,  $R_{in} = 50 \Omega$ ,  $C_1 = C_i = 0.1 \mu\text{F}$ ,  $R_1 = R_2 = R_3 = 100 \text{ k}\Omega$ ,  $R_F = 1 \text{ M}\Omega$ , and supply voltages  $= \pm 15 \text{ V}$ . Determine the bandwidth of the amplifier?
19. In a differential instrumentation amplifier using a transducer bridge,  $R_1 = 1 \text{ k}\Omega$ ,  $R_F = 4.7 \text{ k}\Omega$ ,  $R_A = R_B = R_C = 100 \text{ k}\Omega$ ,  $V_{dc} = +5 \text{ V}$  and supply voltages  $= \pm 15 \text{ V}$ . The transducer is thermistor with following specifications:  $R_T = 100 \text{ k}\Omega$  at a reference temperature of  $25^\circ\text{C}$ , temperature co-efficient of resistance  $= -1 \text{ k}\Omega/^\circ\text{C}$ . Determine the output voltage at  $0^\circ\text{C}$  and at  $100^\circ\text{C}$ .
20. Design a 60 Hz active notch filter?
21. Design a wide band-pass filter with  $f_L = 200 \text{ Hz}$ ,  $f_H = 1 \text{ kHz}$  and a pass band gain of 4. Draw the frequency response plot of this filter. Also calculate the quality factor, Q of the filter?

(5 x 4 = 20)

### Section D

#### Answer any 3 (12 marks each)

- 22.1. With the help of suitable circuit diagrams, derive the expressions for (i) voltage gain (ii) input resistance and (iii) output resistance of a voltage-series feedback amplifier. Explain why the non-inverting amplifier with feedback is called a perfect voltage amplifier?  
**OR**
2. What is an instrumentation amplifier? Explain the working of instrumentation amplifier using Transducer Bridge.
- 23.1. Explain the difference between (i) inverting and differential summing amplifier and (ii) inverting and non-inverting averaging amplifier.  
**OR**
2. (a) Discuss the theory of operation of a first order high pass Butterworth filter using op-amp. (b) Design a high-pass filter at cutoff frequency of 1 kHz with a passband gain of 2. Also plot the frequency response curve.
- 24.1. With necessary theory and circuit diagrams, explain the working of (a) wide band-pass filter and (b) a narrow band-pass filter?  
**OR**
2. (a) With the help of suitable diagrams, explain the working of a square-wave generator using op-amp. (b) Design a square wave oscillator, so that  $f_o = 1 \text{ kHz}$ . The op-amp is a 741 with dc supply voltages  $= \pm 15 \text{ V}$ .

(12 x 3 = 36)