B. Sc. DEGREE END SEMESTER EXAMINATION MARCH - 2020

SEMESTER – 4: PHYSICS (CORE COURSE)

COURSE: 15U4CRPHY4 – ELECTRICITY AND ELECTRODYNAMICS

(For Regular - 2018 Admission and Supplementary / Improvement 2017, 2016, 2015,2014 Admissions)

Time: Three Hours

PART A (Very short answer questions)

Answer **all** questions. Each question carries **1** Mark

- 1. Define time constant of a CR circuit and its importance.
- 2. Give the growth curve of LR circuit for small and large time constant.
- 3. Compare peak factor and form factor of ac.
- 4. What do you mean by the resonant frequency of a circuit?
- 5. What is Thevenin's theorem?
- 6. Give the work done to move a charge in an electric field.
- 7. What is magnetic vector potential?
- 8. Give the equation of continuity and explain the terms. (1 x 8 = 8)

PART B (Short answer)

Answer any Six questions. Each question carries 2 Marks

- 9. Explain the expression for the decay of current in an L-R circuit at any instant t and obtain the graphical variation.
- 10. Explain critical discharging of a capacitor in an LCR circuit and plot the charge-time curve.
- 11. Compare ideal constant voltage source and current source.
- 12. Explain the electric potential of a continuous charge distribution.
- 13. Obtain Poisson's and Laplace's equations.
- 14. Explain Biot-Savart Law.
- 15. How did Maxwell fix the Ampere's law?
- 16. Define Poynting vector.

PART C (Problem/Derivations)

Answer **any Four** question. Each question carries **5** Marks

- 17. Show that charge flowing through the coil of a Ballistic Galvanometer is proportional to first ballistic throw and hence define ballistic reduction factor.
- 18. Find the value of the time constant in an L-R circuit when the current rises to 63.2% of its steady value in one second.

Max. Marks: 60

(2 x 6 = 12)

20U420

- An alternating emf 220 volts 50 cps is applied to a circuit containing an inductance of 0.5H, a capacitor 15μF and a resistance 100ohms in series. Find the current and the phase lag.
- 20. The atomic number of lead is 82 and the charge of the proton is 1.6x10⁻¹⁹C. Calculate the electric potential at the surface of nucleus of lead if the nuclear radius is 6.6 x 10⁻¹⁵m.
- 21. Derive the magnetic field due to current I in a straight wire.
- 22. Derive the Maxwell's equations in matter. (5 x 4 = 20)

PART D (Long answer questions)

Answer any Two question. Each question carries 10 Marks

- 23. With necessary theory, circuits and graph discuss the discharging of a capacitor through a resistance and inductance and discuss the special cases.
- 24. Discuss in detail the theory and experiment to measure high resistance by the leakage method.
- 25. Derive the electrostatic energy stored in a continuous charge distribution and state and prove the Poynting's theorem.
- 26. a) Derive the energy and momentum of electromagnetic waves b) Give an account on the experimental method for the production and detection (Hertz experiment) of electromagnetic waves.(10 x 2 = 20)
