Reg. No	Name	23U111
keg. No	Name	23011

B.C.A DEGREE END SEMESTER EXAMINATION : NOVEMBER 2023 SEMESTER 1 : MOBILE APPLICATIONS AND CLOUD TECHNOLOGY

COURSE: 19U1CRBCA1: COMPUTER FUNDAMENTALS AND ORGANISATION

(For Regular 2023 Admission and Improvement/Supplementary 2022/2021 Admissions)

Answer All (1 mark each)

PART A

- 1. Convert (110011.1001)2 to decimal.
- 2. Is Google a web server? Justify your answer.
- 3. List the fields in an instruction.
- Define latches.

Time: Three Hours

- 5. Define enable inputs.
- 6. List the functional units of a computer.
- 7. Which gates are used in parity checking and parity generation of binary numbers?
- 8. Write an example for register addressing mode.
- 9. What is a trigger?
- 10. Find the BCD of (25)10

 $(1 \times 10 = 10)$

Max. Marks: 75

PART B

Answer any 8 (2 marks each)

- 11. Differentiate WAN and MAN.
- 12. Simplify Commutative law with truth table and logical circuits.
- 13. What is direct addressing mode? Write the syntax and example.
- 14. Simplify [(A+B)'+C'] ' using Demorgans theorem.
- 15. List the draw backs of second generation computers.
- 16. What are the various methods used for triggering flip-flops?
- 17. What do you mean by a latch? Why that name?
- 18. Subtract 7654 34562 using BCD.
- 19. Subtract (AB16-45DA)16.
- 20. What is register addressing mode? Write the syntax and example.

 $(2 \times 8 = 16)$

PART C

Answer any 5 (5 marks each)

- 21. Differentiate half adder and full adder.
- 22. Convert POS expressionF(X,Y,Z) = (X'+Y'+Z).(X+Y+Z).(X+Y+Z') to SOP expression.
- 23. Prove NAND gate is a universal gate.
- 24. Explain about multiplexers and draw 4:1 mux.
- 25. Explain BCD with its advantage and disadvantage. Perform 243 412 and 599 + 984 using BCD.
- 26. Explain the classification of instruction format of a microprocessor.
- 27. Explain the functional units of computer.

 $(5 \times 5 = 25)$

PART D Answer any 2 (12 marks each)

- 28. Discuss about demultiplexers and draw a 1:8 demux with enable inputs.
- 29. Explain muliplexers and demultiplexers and draw any mux and demux.
- 30. Define K-map and don't care condition. Simplify using K-map. a) $F(N,X,Y,Z)=\sum(0,1,2,3,5,7,8,9,10,12,13)$ b) $F(X,Y,Z,W)=\sum M(0,2,6,10,11,12,13)$ and $dc(X,Y,Z,W)=\sum M(3,4,5,14,15)$ c) $F(a,b,c,d)=\sum(0,1,3,4,5,6,7,13,15)$
- 31. Describe the applications of computer in the field of data processing, information processing and office automation.

 $(12 \times 2 = 24)$